

## Hw 4

Question1:

HW 4

Alejandro Sherman

#1 For the RC circuit shown below, the required arrival times at node 1 and 2 are respectively 2ns and 1.2ns.

a) Compute the required arrival time at the source node 0.

$$T_{\text{source}} = \min(T_1 - D_1) = \min(T_1 - D_1, T_2 - D_2)$$

$$D_1 = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6 + C_7 + C_8) + R_2(C_2 + C_3 + C_4 + C_5) + R_3(C_3 + C_4 + C_5) + R_4(C_4 + C_5) + R_5 C_5$$

$$= 10 \times 19 + 60 \times 12 + 60 \times 9 + 60 \times 6 + 60 \times 3 = 1990 \text{ ps}$$

$$D_2 = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6 + C_7 + C_8) + R_6(C_6 + C_7 + C_8) + R_7(C_7 + C_8) + R_8 C_8$$

$$= 10 \times 19 + 80 \times 6 + 80 \times 4 + 80 \times 2$$

$$= 1150 \text{ ps}$$

$$1n = 1000 \text{ p}$$

$$T_{\text{source}} = \min(2000 - 1990, 1200 - 1150)$$

$$10 \text{ ps}$$

$$50 \text{ ps}$$

$$T_{\text{source}} = 10 \text{ ps}$$

b) If we insert one buffer with  $C_{\text{buf}} = 2 \text{ pF}$ ,  $R_{\text{buf}} = 10 \Omega$  and  $D_{\text{buf}} = 5 \text{ ps}$  at node 1, what is the new required arrival time at node 0?

$$\text{updated } D_1 = R_1(C_1 + C_{\text{buf}} + C_6 + C_7 + C_8) + R_2(C_{\text{buf}}) + D_{\text{buf}} + R_{\text{buf}}(C_2 + C_3 + C_4 + C_5) + R_3(C_3 + C_4 + C_5) + R_4(C_4 + C_5) + R_5 C_5$$

$$= 10 \times 9 + 60 \times 2 + 5 + 10 \times 12 + 60 \times 9 + 60 \times 6 + 60 \times 3$$

$$= 1415 \text{ ps}$$

$$\text{updated } D_2 = R_1(C_1 + C_{\text{buf}} + C_6 + C_7 + C_8) + R_6(C_6 + C_7 + C_8) + R_7(C_7 + C_8) + R_8 C_8$$

$$= 10 \times 9 + 80 \times 6 + 80 \times 4 + 80 \times 2$$

$$= 1050 \text{ ps}$$

$$T_{\text{source}} = \min(2000 - 1415, 1200 - 1050)$$

$$585$$


$$150$$

$$T_{\text{source}} = 150 \text{ ps}$$

Question2:

Question #2

 a) Draw the schematic of the logic circuit described by the given verilog:



b) What is the critical path of this design from primary inputs to outputs and what is the delay of the critical path in terms of unit delay?

Critical path:

a → xor → not → and → or → y    Delay = 2 + 1 + 3 + 3 = 9

b → xor → not → and → or → y    Delay = 2 + 1 + 3 + 3 = 9

Question 3:

Notice that the logic below consists of three repeated parts.

(a) Write a Verilog explicit structural description of the logic which consists of two modules, one module, name it part-logic, will be for the part that's repeated, the other, name it whole-logic, will instantiate part-logic three times and interconnect them appropriately. Write the part-logic using the Verilog primitives. Choose appropriate inputs and outputs for the two modules based on the diagram.

a) part-logic

```
module part-logic( x, y, a, b, c);
    input a, b, c;
    wire t1;
    output x, y;
    not n1(t1, b);
    and a1(x, a, t1);
    or o1(y, c, x);
endmodule
```

whole-logic

```
module whole-logic( x, y, a, b, c);
    input [2:0] a;
    input [2:0] b;
    input c;
    wire t1, t2;
    output [2:0] x;
    output y;
    part-logic pl1(x[0], t1, a[0], b[0], c);
    part-logic pl2(x[1], t2, a[1], b[1], t1);
    part-logic pl3(x[2], y, a[2], b[2], t2);
endmodule
```

(b) Repeat (a) by writing the part-logic using the continuous assignment statement.

b) part-logic

```
module part-logic( x, y, a, b, c);
    input a, b, c;
    output x, y;
    assign x = a & (~b);
    assign y = c | x;
endmodule
```

Question 4: Modified code from lecture slides

```
module xor8(xout, xin1, xin2);
output [1:8] xout;
input [1:8] xin1, xin2;
    xor (xout[8], xin1[8], xin2[8]),
        (xout[7], xin1[7], xin2[7]),
        (xout[6], xin1[6], xin2[6]),
        (xout[5], xin1[5], xin2[5]),
        (xout[4], xin1[4], xin2[4]),
        (xout[3], xin1[3], xin2[3]),
        (xout[2], xin1[2], xin2[2]),
        (xout[1], xin1[1], xin2[1]);
endmodule
```

```
module deMux(outVector, a, b, c, d, enable);
output [1:8] outVector;
input      a, b, c, d enable;
    and (m12, d, c, ~b, ~a, enable),
        (m11, d, ~c, b, a, enable),
        (m10, d, ~c, b, ~a, enable),
        (m9, d, ~c, ~b, a, enable),
        (m7, ~d, c, b, a, enable),
        (m6, ~d, c, b, ~a, enable),
        (m5, ~d, c, ~b, a, enable),
        (m3, ~d, ~c, b, a, enable);

    assign outVector = {m3, m5, m6, m7, m9, m10, m11, m12};
endmodule
```

```
module hamEncode(vIn, valueOut);
input [1:8] vIn;
output [1:12] valueOut;
wire [1:12] swap;
wire h1, h2, h4, h8, hold;

    xor (h1, vIn[1], vIn[2], vIn[4], vIn[5], vIn[7]),
        (h2, vIn[1], vIn[3], vIn[4], vIn[6], vIn[7]),
        (h4, vIn[2], vIn[3], vIn[4], vIn[8]),
        (h8, vIn[5], vIn[6], vIn[7], vIn[8]);

    assign swap = {h1, h2, vIn[1], h4, vIn[2:4], h8, vIn[5:8]};
    assign hold = ^swap;
    assign valueOut = {swap, hold};
endmodule
```

```
module hamDecode(vIn, valueOut, doubleerror);
input [1:12] vIn;
output [1:8] valueOut;
wire c1, c2, c4, c8;
wire [1:8] bitflippers
    xor (c1, vIn[1], vIn[3], vIn[5], vIn[7], vIn[9], vIn[11]),
        (c2, vIn[2], vIn[3], vIn[6], vIn[7], vIn[10], vIn[11]),
        (c4, vIn[4], vIn[5], vIn[6], vIn[7], vIn[12]),
```

```

        (c8, vln[8], vln[9], vln[6], vln[7], vln[12]);

    deMux mux1 (bitFlippers, c1, c2, c4, c8, 1'b1);
    xor8 x1 (valueOut, bitFlippers, {vln[3], vln[5], vln[6], vln[7], vln[9], vln[10], vln[11], vln[12]});
    assign doubleerror = ~(^ (vln & (c1 | c2 | c4 | c8)));
endmodule

module testHam();
reg  [1:8] original;
wire [1:8] regenerated;
wire [1:12] encoded;
            messedUp;
wire [1:13] thirteenth;
integer    seed;

    initial begin
        seed = 1;
        forever begin
            original = $random (seed);
            thirteenth = $random (seed) & 13'b 0000_0000_0000_0000_1;
            #1
            $display ("original=%h, encoded=%h, thirteenth=%h, doubleerror=%h,
            messed=%h, regen=%h", original, encoded, thirteenth, doubleerror,
            messedUp, regenerated);
        end
    end
    hamEncode hIn(original, encoded);
    hamDecode hOut(messedUp, regenerated, doubleerror);

    assign messedUp = encoded ^ 12'b 0000_0010_0000 ^ thirteenth;
endmodule

```