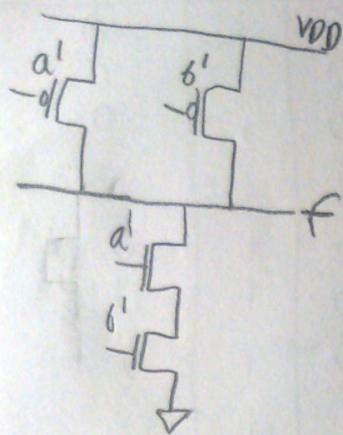



HW2 Problem 1 Design complementary gates for the following: Inverted inputs allowed!

a)  $a+b' f = (a'b')'$



Truth Table		Out	$a'b'$
A	B		
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	0


b)  $a'b f = (a'+b')'$

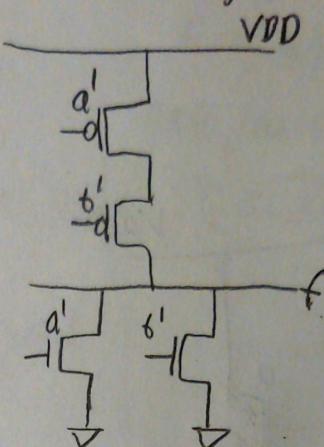


A	B	Out	$a'+b'$
0	0	0	1
0	1	0	0
1	0	0	0
1	1	1	0

c)  $(a+b)c f = ((a'b')'+c')$

Truth Table		Out	$a'b'+c'$
A	B		
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

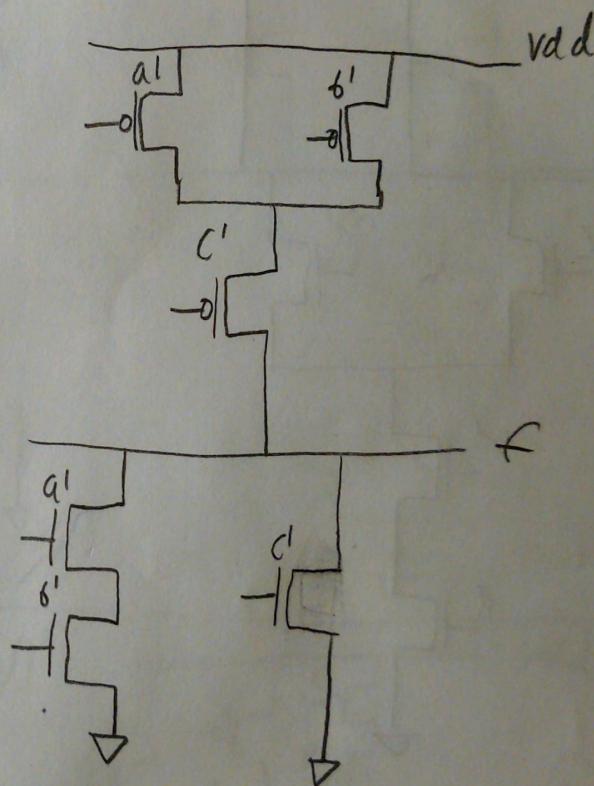
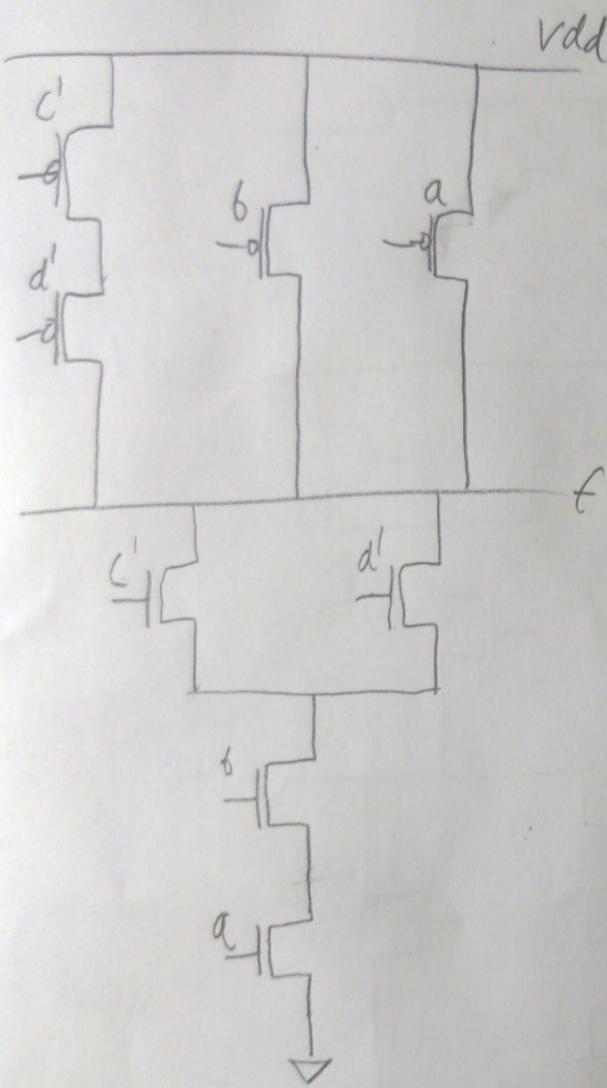
$$d) (ab)' + (cd) \stackrel{aet}{=} a' + b' + (cd) f = (a \cdot b \cdot (c'd' + d'))'$$



A	B	C	D	$(AB)'$	$CD$	Out	$a \cdot b \cdot (c'd' + d')$
0	0	0	0	1	0	1	0
0	0	0	1	1	0	1	0
0	0	1	0	1	0	1	0
0	0	1	1	1	1	1	0
0	1	0	0	1	0	1	0
0	1	0	1	1	0	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	0
1	0	1	1	1	1	1	0
1	1	0	0	0	0	0	1
1	1	0	1	0	0	0	1
1	1	1	0	0	0	0	1
1	1	1	1	0	1	1	0


Question 2

Write the logic expression and draw transistor level schematic


a) AOI32

$$f = (abc + de)'$$

gate logic:

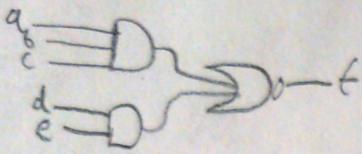

Transistor level:

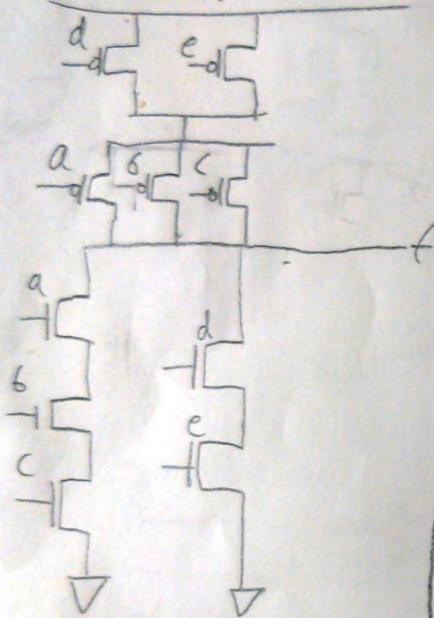


b) AOI312

$$f = (abc + d + ef)'$$

gate logic:




Transistor level: vdd

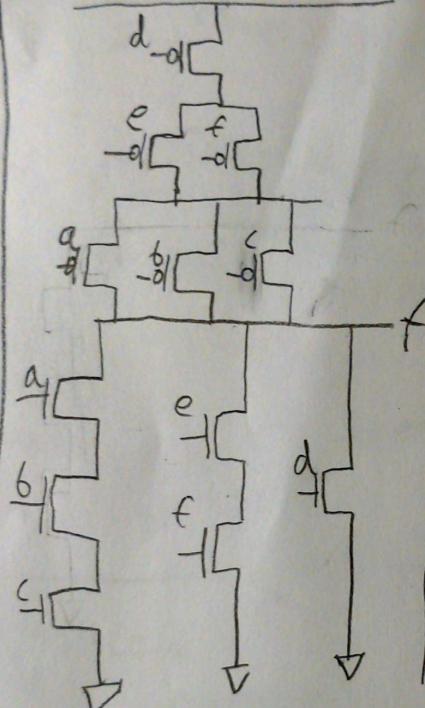


c) OAII22

$$f = [(a+b)(c+d)]'$$

gate logic

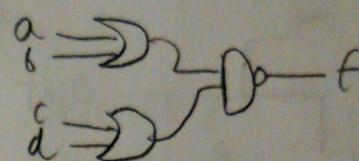


Transistor level:

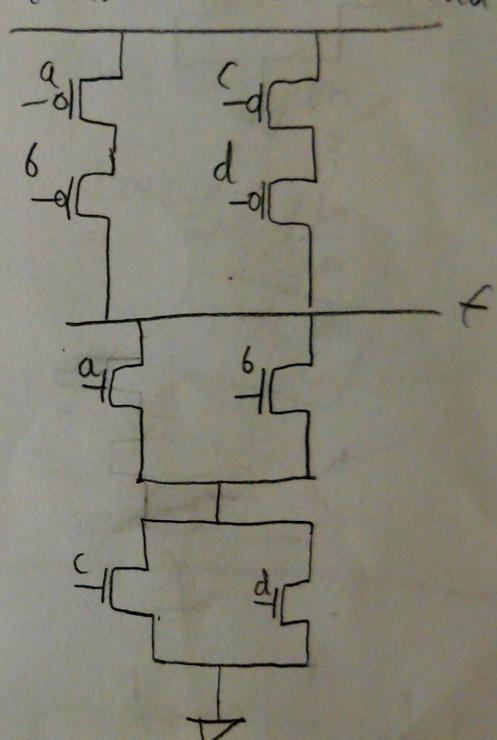


d) OAII323

$$f = [(a+b+c)(d+c)(f+g+h)]'$$


gate logic

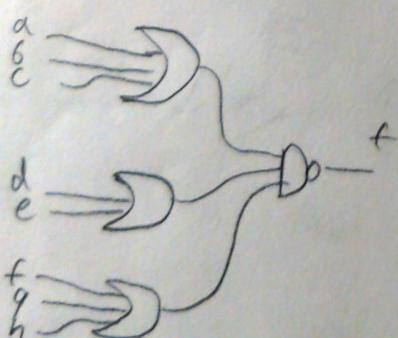

Transistor level:

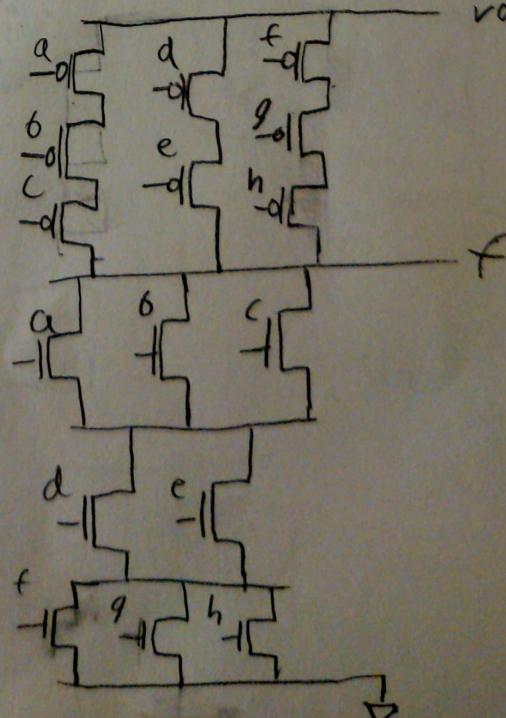

Question 3: Draw the circuit level schematic. Write logic

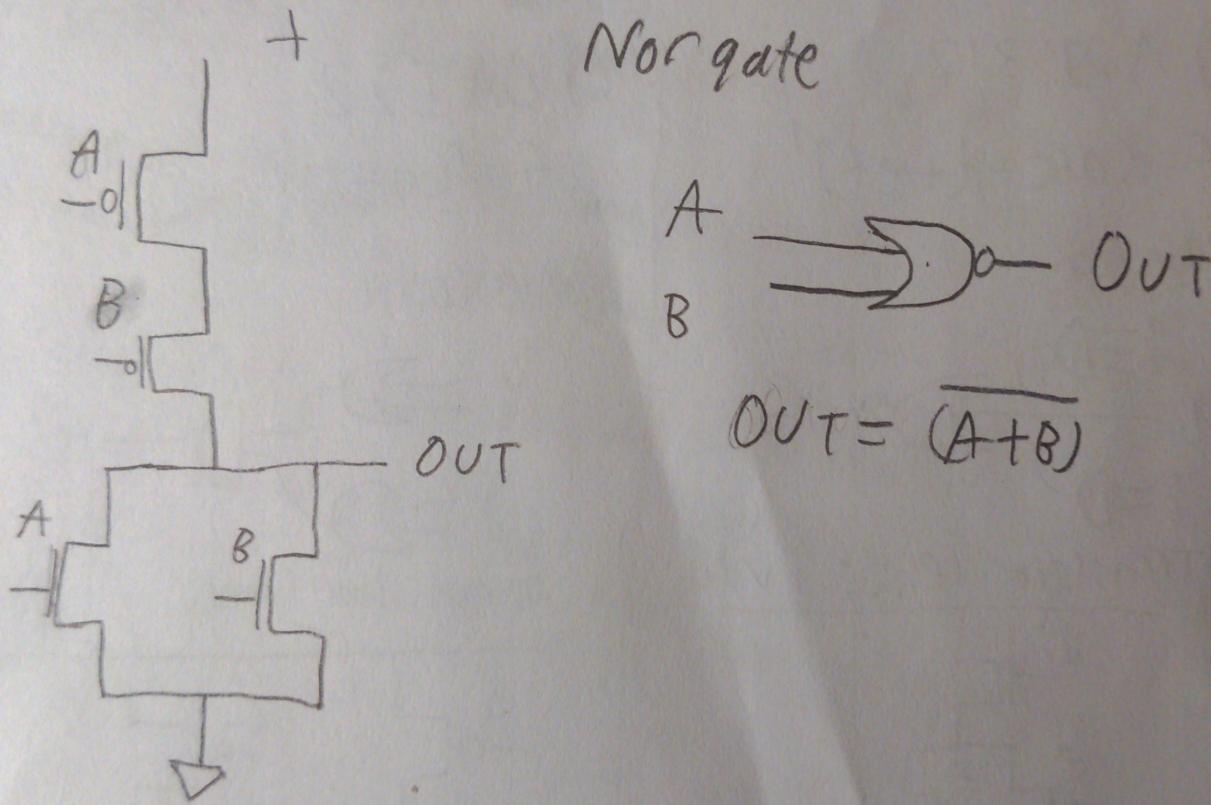

Problem 4: Size the transistors so the pullup and pulldown are approximately equal


$$NMOS\ R_n = 6.47k\Omega, PMOS\ R_p = 29.6k\Omega \quad CL$$

$$R_p = 4.5 \cdot R_n \text{ from lecture!}$$

\* assume all PMOS has the same  $W_P$  and  $L_P$

$$\text{delay} = (R_p + R_C)C = (R_{down} + R_L)C$$

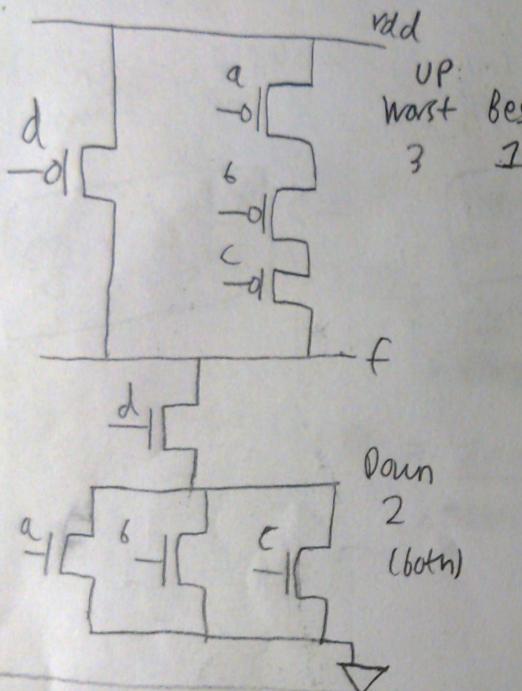a)  $f = a'b'c' + d' = ((a+b+c)d)'$  Worst case



$$R_p = \frac{3 \times L_P}{W_P} \times R_p$$

$$R_{down} = 2 \times \frac{L_n}{W_n} \times R_n$$

Best case

$$R_p = 1 \times \frac{L_P}{W_P} \times R_p$$

$$R_{down} = 2 \times \frac{L_n}{W_n} \times R_n$$


$$3 \times 4.5 \frac{L_P}{W_P} = 2 \frac{L_n}{W_n}$$

$$\Rightarrow \frac{W_P}{L_P} = 6.75 \times \frac{W_n}{L_n}$$

$$1 \times 4.5 \frac{L_P}{W_P} = 2 \frac{L_n}{W_n}$$

$$\Rightarrow 2.25 \frac{W_n}{L_n}$$

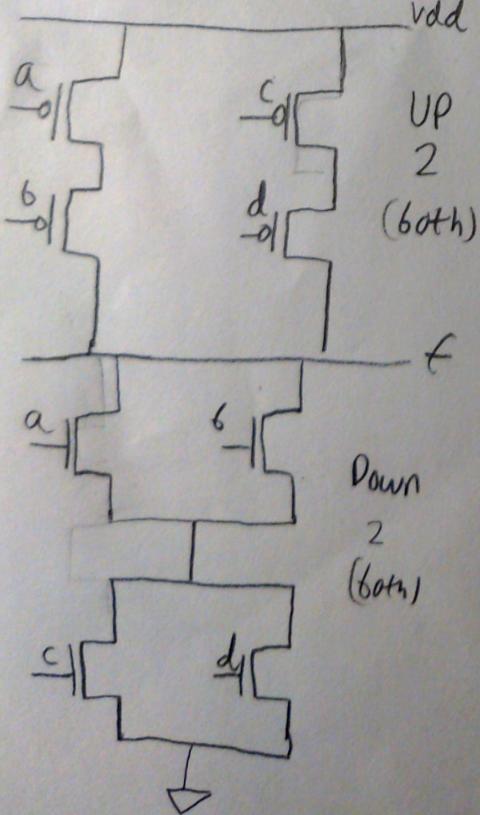b)  $F = a'b' + c'd' = ((a+b) \cdot (c+d))'$



worst case

$$R_p = 2 \times \frac{L_P}{W_P} \times R_p$$

$$R_{down} = 2 \times \frac{L_n}{W_n} \times R_n$$


Best case is the same!

$$\frac{W_P}{L_P} = 4.5 \frac{W_n}{L_n}$$

$$2 \times 4.5 \frac{L_P}{W_P} = 2 \frac{L_n}{W_n}$$

$$\Rightarrow \frac{W_P}{L_P} = 4.5 \frac{W_n}{L_n}$$
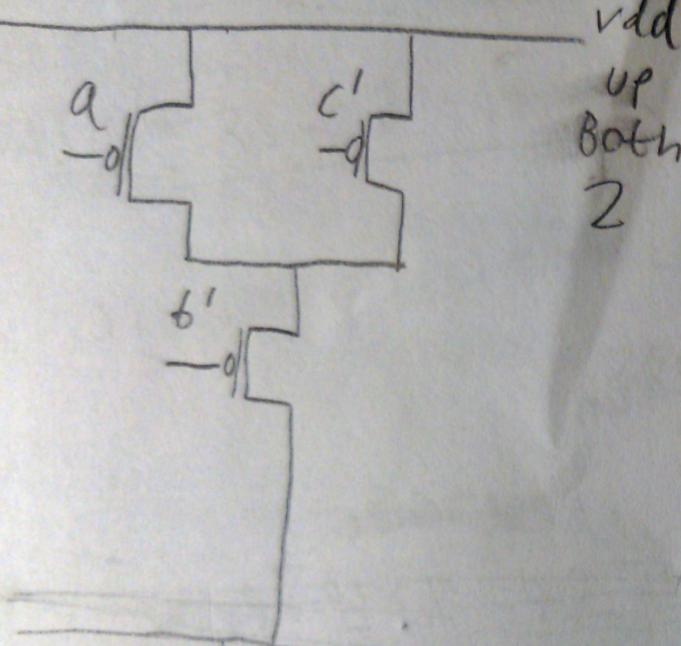
$$f = a'b + bc = b(a' + c) = (b' + ac')' \text{ assuming inverted inputs come from direct inputs without needing an inverter}$$



vdd

up

Both

2

Worst case

$$R_{up} = \frac{2 \cdot L_p}{W_p} \times R_p$$

$$R_{down} = 2 \times \frac{L_n}{W_n} \times R_n$$

Best case:

$$R_{up} = 2 \frac{L_p}{W_p} \times R_p$$


$$R_{down} = 1 \times \frac{L_n}{W_n} \times R_n$$

$$2 \times 4,5 \frac{L_p}{W_p} = 2 \frac{L_n}{W_n}$$

$$\Rightarrow \boxed{\frac{W_p}{L_p} = 4,5 \frac{W_n}{L_n}}$$

$$2 \times 4,5 \frac{L_p}{W_p} = 1 \frac{L_n}{W_n}$$
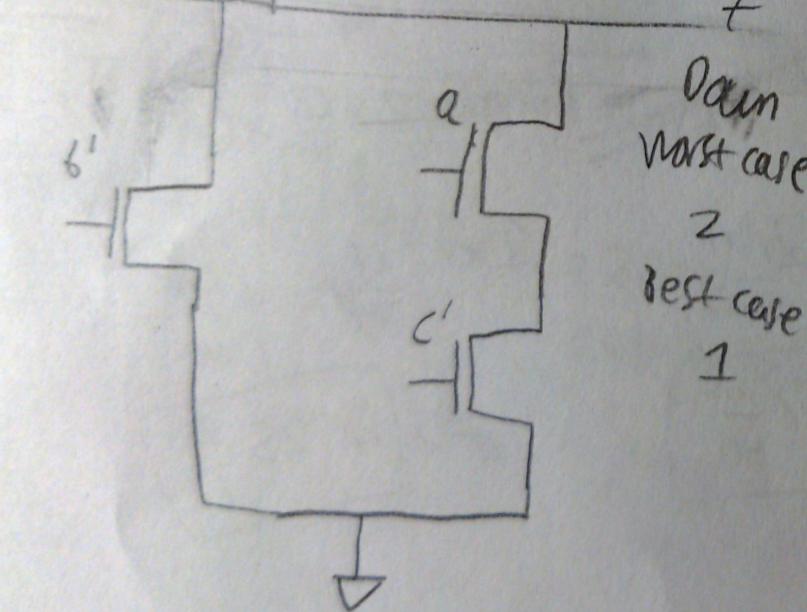
$$\Rightarrow \boxed{\frac{W_p}{L_p} = 9 \frac{W_n}{L_n}}$$



Open  
Worst case

2

Best case  
1

Question 5: Compute the value of  $R_{eff}$  required to model an inverter that

reaches 50% of its output value at 20ps with load  $C_L$  equal to  $3C_1$ ,  $4C_1$  and  $5C_1$ .

What effect does load capacitance have on the effective resistance ( $C_1 = 0.89 \times 10^{-15} F$ )?

$$R_n = 6.47 k\Omega \quad PMOS = 29.6 k\Omega \quad NMOS \quad R_n = 6.47 k\Omega \quad C_1 = 0.89 \times 10^{-15} F$$

$$\text{Load } 3C_1 \quad C_L = 3 \times 0.89$$

$$R_{eff} = \frac{t_s}{C_L \times \ln(\frac{V_{dd}}{V_{dd}-V_{out}})} = \frac{20 \times 10^{-12}}{0.89 \times 3 \times \ln(\frac{1}{2}) \times 10^{-15}} = 10.81 \times 10^3 \Omega$$

As load capacitance increases,  
the effective resistance  
decreases.

$$\text{Load } 4C_1 \quad C_L = 4 \times 0.89 = \frac{20 \times 10^{-12}}{0.89 \times 4 \times \ln(\frac{1}{2}) \times 10^{-15}} = 8.11 \times 10^3 \Omega$$

$$\text{Load } 5C_1 \quad C_L = 5 \times 0.89 = \frac{20 \times 10^{-12}}{0.89 \times 5 \times \ln(\frac{1}{2}) \times 10^{-15}} = 6.48 \times 10^3 \Omega$$


Question 6: Compute transition times for a four input NAND gate with 8/2 pulldown

$$R_n = 6.47 \text{ k}\Omega$$

$$\frac{W}{L} = \frac{8}{2}$$

for n-type.  $\frac{1}{2}$  pullup that drives NOR four input

Four input NAND

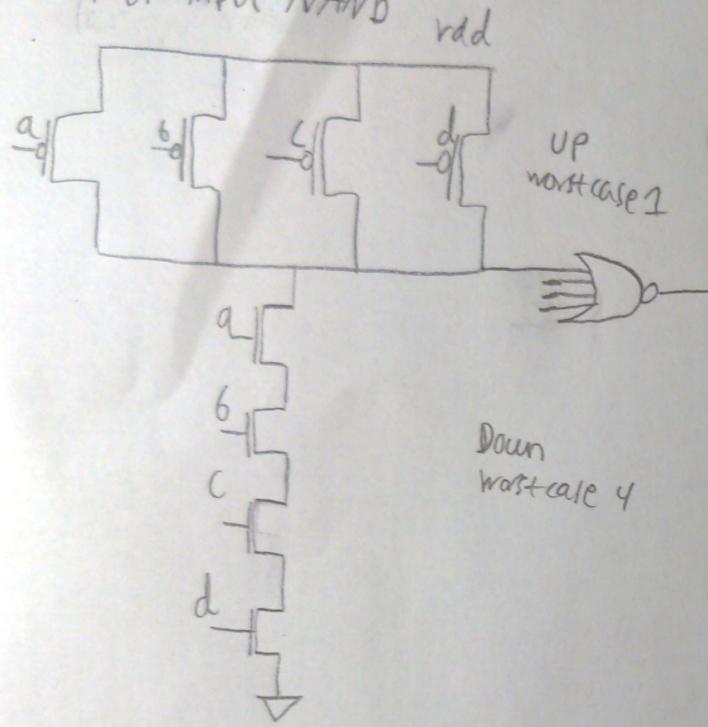

$$\text{fall time } t_f = 2.3 \times (R_{\text{down}} + R_L) C_L$$

$$\text{rising time } t_r = 2.3 \times (R_{\text{up}} + R_E) C_L$$

$$R_{\text{down}} = 4 \times \frac{L_n}{W_n} \times R_n = 4 \times \frac{2}{8} \times 6.47 \text{ k}\Omega = 6.47 \text{ k}\Omega$$

$$R_{\text{up}} = 1 \times \frac{L_n}{W_n} \times R_P = 1 \times \frac{2}{8} \times 29.6 \text{ k}\Omega = 7.4 \text{ k}\Omega$$

$$C_L = \sum_{i=0}^N \frac{W_i}{L_i} C_L$$

$$C_L = \frac{8}{2} C_L + \frac{8}{2} C_L$$

$$= 4 C_L + 4 C_L = 8 C_L = 8 \times 0.89 \text{ fF}$$

$$R_L = 0 \quad = 7.12 \times 10^{-15} \text{ F}$$

$$t_f = 2.3 \times 6.47 \times 10^{-10} \times 10^3 \times 7.12 \times 10^{-15} = 106 \text{ ps}$$

$$t_r = 2.3 \times 7.4 \times 10^{-10} \times 7.12 \times 10^{-15} = 121 \text{ ps}$$

Question 7

$$\lambda = 90\text{nm} = 0.09\mu\text{m}$$

Poly resistance:  $\frac{8\Omega}{\square}$   
Metal1 resistance:  $0.08\frac{\Omega}{\square}$

a) Poly wire

compute rise time for a two-input NAND gate with 8/2 pulldown and 8/2 pullup that drives these wires (assume that the unit impedances are modeled as single lump)

with width  $3\lambda$ , length  $300\lambda$

$$R_L = \frac{L}{W} \times r_{poly} = \frac{300\lambda}{3\lambda} \times 8\frac{\Omega}{\square} = 800\Omega$$

$$R_{up} = \frac{L_p}{W_p} \times R_p = \frac{2}{8} \times 29.6k\Omega = 7.4k\Omega$$

$$t_r = 2.3 \times (7.4 \times 10^3 + 0.8 \times 10^3) \times 3.899 \times 10^{-15}\text{F}$$

$$= 7.35 \times 10^{-11}\text{s} = \boxed{73.5\text{ps}}$$

$$C_r = C_{plate} + C_{fringe}$$

$$A_c \times C_{plate-unit} + P_c \times \frac{C_{fringe-unit}}{63 \times 10^{-18}} \text{ plus in } \lambda = 0.09\mu\text{m}$$

$$= 3\lambda \times 300\lambda \times 63 \times 10^{-18} + (3\lambda + 300\lambda) \times 2 \times 63 \times 10^{-18}$$

$$= 4.59 \times 10^{-16} + 3.44 \times 10^{-15}$$

$$= \boxed{3.899 \times 10^{-15}\text{F}}$$

b) Metal1 wire of width  $4\lambda$  length  $600\lambda$

$$R_i = \frac{L}{W} \times r_{metal1} = \frac{600\lambda}{4\lambda} \times 0.08\frac{\Omega}{\square} = 12\Omega$$

$$R_{up} = \frac{L_p}{W_p} \times R_p = \frac{2}{8} \times 29.6k\Omega$$

$$= 7.4k\Omega$$

$$C_r = C_{plate} + C_{fringe}$$

$$A_c \times C_{plate-unit} + P_c \times \frac{C_{fringe-unit}}{54 \times 10^{-18}}$$

$$= 4\lambda \times 600\lambda \times 36 \times 10^{-18} + (4\lambda + 600\lambda) \times 2 \times 54 \times 10^{-18}$$

$$t_r = 2.3 \times (7.4 \times 10^3 + 12) \times 6.5698 \times 10^{-15}$$

$$= 6.998 \times 10^{-16} + 5.87 \times 10^{-15}$$

$$= 1.119 \times 10^{-10} = \boxed{111.9\text{ps}}$$

$$= 6.5698 \times 10^{-15}$$

c) Metal 2 wire of width  $w = 4\lambda$ , length  $1200\lambda$

$$R_L = \frac{L}{w} \times \frac{\rho_{\text{metal 2}}}{D} = \frac{1200\lambda}{4\lambda} \times 0.08 \frac{\Omega}{\Omega} = 24 \Omega$$
$$R_{UP} = \frac{L_P}{w_P} \times R_P = \frac{2}{8} \times 29.6 \text{ k}\Omega$$
$$= 7.4 \text{ k}\Omega$$

$$C_L = C_{\text{plate}} + C_{\text{frame}}$$

$$A_{ex} = C_{\text{plate}} - \text{unit}$$

$$\begin{aligned} & \frac{P_{\text{cap}}}{\lambda} = \frac{36 \times 10^{-18}}{51 \times 10^{-18}} + \frac{P_C + f_{\text{frame}} - \text{unit}}{51 \times 10^{-18}} \\ & = 4\lambda \times 1200\lambda \times 36 \times 10^{-18} + (4\lambda + 1200\lambda) \times 2 \times 51 \times 10^{-18} \\ & = 1.4 \times 10^{-15} + 1.105 \times 10^{-14} \\ & = 1.245 \times 10^{-14} \end{aligned}$$

$$\begin{aligned} t_r &= 2.3 \times (7.4 \times 10^3 + 24) \times 1.245 \times 10^{-14} \\ &= 2.126 \times 10^{-10} = \boxed{212.6 \text{ ps}} \end{aligned}$$

Question 8 Metal 2 wire  $R_{int}=500\Omega$   $C_{int}=200fF$

$$R_0 = 6.47k\Omega \quad C_0 = 1.78fF$$

a) If no additional buffer is inserted, then what is 50% delay?

$$\begin{aligned} T_{50\%} &= K [0.7 R_0 \left( \frac{C_{int}}{K} + C_0 \right) + \frac{R_{int}}{K} (0.4 \frac{C_{int}}{K} + 0.7 C_0)] \\ &= 2 \left[ 0.7 \times 6.47 \times 10^3 \times \left( \frac{200 \times 10^{-15}}{2} + 1.78 \times 10^{-15} \right) + \frac{500}{2} (0.4 \times \frac{200 \times 10^{-15}}{2} + 0.7 \times 1.78 \times 10^{-15}) \right] \\ &= \frac{0.7 \times 6.47 \times 10^3}{2} \times 2.0178 \times 10^{-13} \quad (81.246) \\ &\quad + \frac{9.1386162 \times 10^{-10}}{2} \quad + \frac{4.0623 \times 10^{-11}}{2} \\ &= 9.1386162 \times 10^{-10} \quad + \quad 4.0623 \times 10^{-11} \\ &= 9.545 \times 10^{-10} = \boxed{954.5 \text{ ps}} \end{aligned}$$

b) One buffer is used!

$$\begin{aligned} T_{50\%} &= 2 \left[ 0.7 \times 6.47 \times 10^3 \times \left( \frac{200 \times 10^{-15}}{2} + (1.78 \times 10^{-15}) \right) + \frac{500}{2} (0.4 \times \frac{200 \times 10^{-15}}{2} + 0.7 \times 1.78 \times 10^{-15}) \right] \\ &= 2 \left[ 0.7 \times 6.47 \times 10^3 \times \frac{1.0178 \times 10^{-13}}{2} + \frac{1.03115 \times 10^{-11}}{2} \right] \\ &= 2 \left[ 4.6096162 \times 10^{-10} + 1.03115 \times 10^{-11} \right] \\ &= 2 \left[ 4.713 \times 10^{-10} \right] \\ &= 9.425 \times 10^{-10} = \boxed{942.5 \text{ ps}} \end{aligned}$$

c)  $T = k \ln K$   $\Rightarrow k = \frac{T}{\ln K}$

c)  $K=2$   $h=2$

3.235

$$TS_{0.5} = K \left[ 0.7 \frac{R_o}{h} \left( \frac{C_{int}}{K} + h C_o \right) + \frac{R_{int}}{K} \left( 0.4 \frac{C_{int}}{K} + 0.7 h C_o \right) \right]$$

$$2 \left[ 0.2 \times \frac{6.47 \times 10^3}{2} \left( \frac{200 \times 10^{-15}}{2} + 2 \times 1.78 \times 10^{-15} \right) + \frac{500}{2} \left( 0.4 \times \frac{200 \times 10^{-15}}{2} + 0.7 \times 2 \times 1.78 \times 10^{-15} \right) \right] \\ 0.7 \times \frac{6.47 \times 10^3}{2} (1.0356 \times 10^{-13}) \times 10 + 1.0623 \times 10^{-11}$$

$$2.3451162 \times 10^{-10} + 1.0623 \times 10^{-11}$$

$$= 2.4513 \times 10^{-10} = \boxed{245.1 \text{ ps}}$$

d) Optimal number of buffers, buffer size, and minimum SO<sub>50%</sub> delay?

$$K = \sqrt{\frac{0.4 R_{int} C_{int}}{0.7 R_o C_o}}$$

$$K = \sqrt{\frac{0.4 \times 500 \times 200 \times 10^{-15}}{0.7 \times 6.47 \times 10^3 \times 1.78 \times 10^{-15}}}$$

$$K = \sqrt{41.962} \\ = \boxed{2.227} \text{ Buffer}$$

$$h = \sqrt{\frac{R_o C_{int}}{R_{int} C_o}}$$

$$h = \sqrt{\frac{6.47 \times 10^3 \times 200 \times 10^{-15}}{500 \times 1.78 \times 10^{-15}}}$$

$$\sqrt{1453.93}$$

$$h = \boxed{38.1} \text{ Buffer size}$$

Minimum SO<sub>50%</sub> delay

$$TS_{0.5} = 2.5 \sqrt{R_o C_o R_{int} C_{int}} \\ 2.5 \sqrt{6.47 \times 10^3 \times 1.78 \times 10^{-15} \times 500 \times 200 \times 10^{-15}}$$

$$\sqrt{1.15166 \times 10^{-21}}$$

$$= 2.5 \cdot 3.3936 \times 10^{-11}$$

$$= 8.484 \times 10^{-11} = \boxed{84.8 \text{ ps}}$$